BILL OF MATERIALS

Useless Music Box with Arduino Nano

Rev. 2026-10-20 11 items

View this project on Printables	Buy me a Beer	Join my club for exclusive models

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

CONTROLLER 1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	Arduino Nano V3 ATmega328P CH340 (soldered headers)	**1**	AliExpress Link	Amazon Link	*Upstream BOM: Nano or equivalent. Servos on D2/D3, toggle D4, buzzer D7.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

ELECTRONICS 1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	Nano V3 I/O expansion shield (3-pin servo headers, DC jack)	**1**	AliExpress Link	Amazon Link	*Upstream BOM. Every pin broken out as a G/V/S 3-pin header, so the two servos plug straight in; V/G pins take the battery 5 V. Not the*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

MOTION

1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	MG90S metal-gear micro servo 180 degree	**x2**	AliExpress Link	Amazon Link	*Upstream: 2x MG90S (SG90 fits too). One lifts the lid, one flips the switch.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

POWER

2 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	18650 battery holder shield with 5 V output (USB charge)	**1**	AliExpress Link	Amazon Link	*Upstream: "18650 battery holder" wired from its 5 V output; a boost-type shield is required, a plain holder gives 3.7 V.*
>>	18650 Li-ion cell 3.7 V	**1**	AliExpress Link	Amazon Link	*Upstream BOM. Buy from a reputable seller; shops restrict cell shipping.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

ELECTRONICS 3 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	KCD1 rocker switch 2-pin (main power)	**1**	AliExpress Link	Amazon Link	*Upstream: "flip on/off switch" for main power. Hole size not stated upstream; measure the printed box before buying a different size.*
>>	MTS-102 mini toggle switch (lid)	**1**	AliExpress Link	Amazon Link	*Upstream: toggle on/off switch on the lid, read on D4. 6 mm panel hole; measure the printed lid.*
>>	Passive buzzer 5 V (tone type)	**1**	AliExpress Link	Amazon Link	*Must be passive; driven with tone() on D7.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

HARDWARE

1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	M2 x 4 mm screws (pan or socket head, not countersunk)	**1**	AliExpress Link	Amazon Link	*Upstream: 8 pcs for expansion board and battery holder. Sold in packs; AliExpress listing is a size-variant listing, pick M2 x 4.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

SUPPLIES

1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	Dupont jumper wire set 40-pin M-M / M-F / F-F	**1**	AliExpress Link	Amazon Link	*Buzzer and battery holder wiring.*

BOM	Product/Project: Useless Music Box with Arduino Nano Revision date: 2026-10-20	https://www.printables.com/@TomKnox_1573/models

CONSUMABLES 1 items

	Description	Qty	AliExpress	Amazon (Geniuslink)	Notes
>>	PLA filament 1.75 mm 1 kg	**1**	AliExpress Link	Amazon Link	*About 5 hours of printing. Printed parts are not purchase rows.*